

② Booth Multiplier:

In this I have created 2 states
state = 0 & 1
for state 0, I calculated ~~both~~ partial
product and In state 1, ~~the~~ I have
added both partial product and stored in
result.

$$\begin{array}{r} a_3 \ a_2 \ a_1 \ a_0 \\ \times \ b_3 \ b_2 \ b_1 \ b_0 \\ \hline \end{array}$$

Here $P1P0 = \left\{ \begin{array}{l} 0 \\ A \\ 2A \\ 4A - A \end{array} \right.$ $\begin{array}{l} b_1 b_0 = 00 \\ b_1 b_0 = 01 \\ b_1 b_0 = 10 \\ b_1 b_0 = 11 \end{array}$

and $P3P2 = \left\{ \begin{array}{l} 0 \\ A \\ 2A \\ 4A - A \end{array} \right.$ $\begin{array}{l} b_3 b_2 = 00 \\ b_3 b_2 = 01 \\ b_3 b_2 = 10 \\ b_3 b_2 = 11 \end{array}$

At And then shifted the 6 bits of $P3P2$
by 2 bits and added this partial product